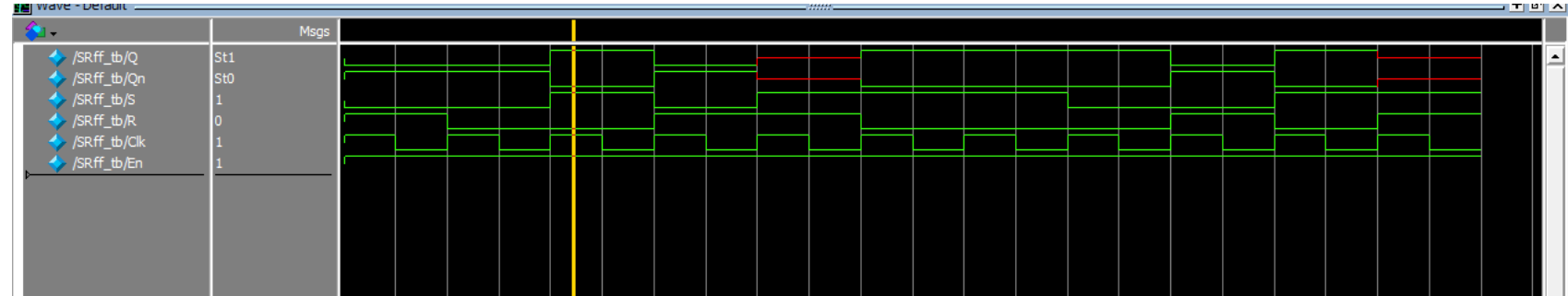


Homework 5

Pranav Nadimpalli


SR Testing Waveform + Transcript

```
run
# Time Clk En S R Q Qn
run
# 20 1 1 0 0 0 1
run
# 30 0 1 0 0 0 1
run
# 40 1 1 1 0 1 0
run
# 50 0 1 1 0 1 0
run
# 60 1 1 0 1 0 1
run
# 70 0 1 0 1 0 1
run
# 80 1 1 1 1 x x
run
# 90 0 1 1 1 x x
run
# 100 1 1 1 0 1 0
run
# 110 0 1 1 0 1 0
run
# 120 1 1 1 0 1 0
run
# 130 0 1 1 0 1 0
run
# 140 1 1 0 0 1 0
run
# 150 0 1 0 0 1 0
run
# 160 1 1 0 1 0 1
run
# 170 0 1 0 1 0 1
run
# 180 1 1 1 0 1 0
run
# 190 0 1 1 0 1 0
run
# 200 1 1 1 1 x x
VSIM 43> run
# 210 0 1 1 1 x x
VSIM 43>
```




JK Testing Waveform + Transcript
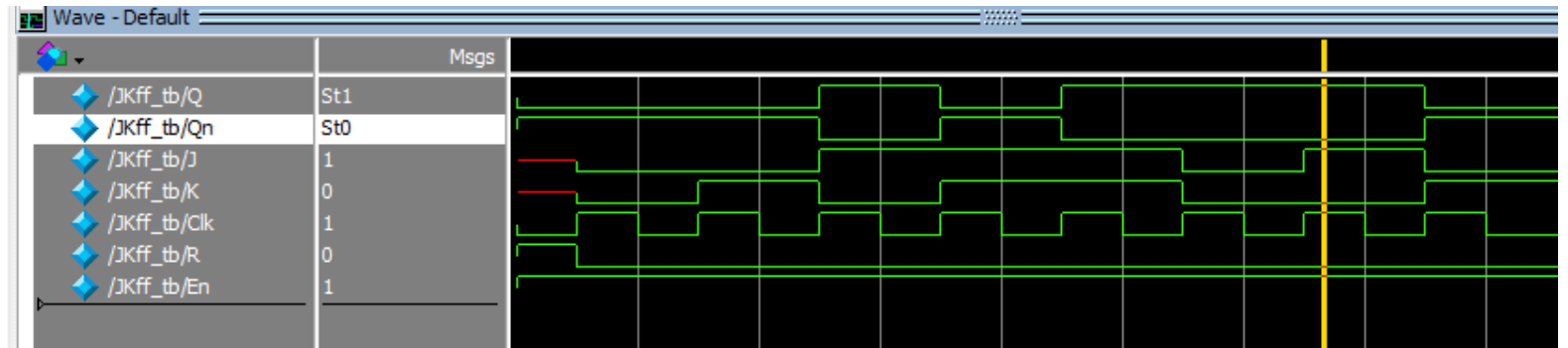
```
add wave position end sim/0Kff_tb/En
VSIM 52> run
# Time J K R Q Qn
run
# 10 0 0 0 0 1
run
run
# 30 0 1 0 0 1
run
run
# 50 1 0 0 1 0
run
run
# 70 1 1 0 0 1
run
run
# 90 1 1 0 1 0
run
run
# 110 0 0 0 1 0
run
run
# 130 1 0 0 1 0
run
run
# 150 0 1 0 0 1
run
run
run
run
VSIM 53> run
```




T Testing Waveform + Transcript
 
```
add wave -position end $Sim:/t_ff_tb/En
VSIM 61> run
# Time T      Q*      Qn*
run
# 10  0      0      1
run
run
# 30  1      1      0
run
run
# 50  0      1      0
run
run
# 70  1      0      1
run
run
VSIM 62> run
```



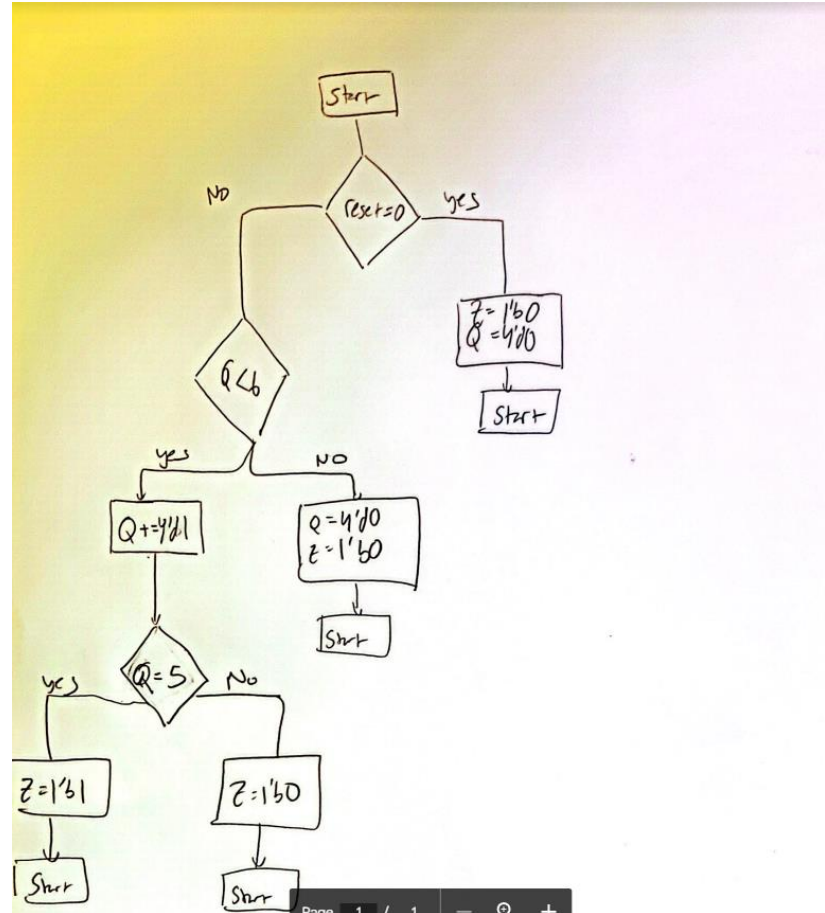Problem 6 Flow Diagram

We evaluate $Q=5$ so we can get $Z=1'b1$ output when $Q=6$




Waveforms & Transcript for Problem 6 and 7

Q6 and Z6 correspond to output for problem 6

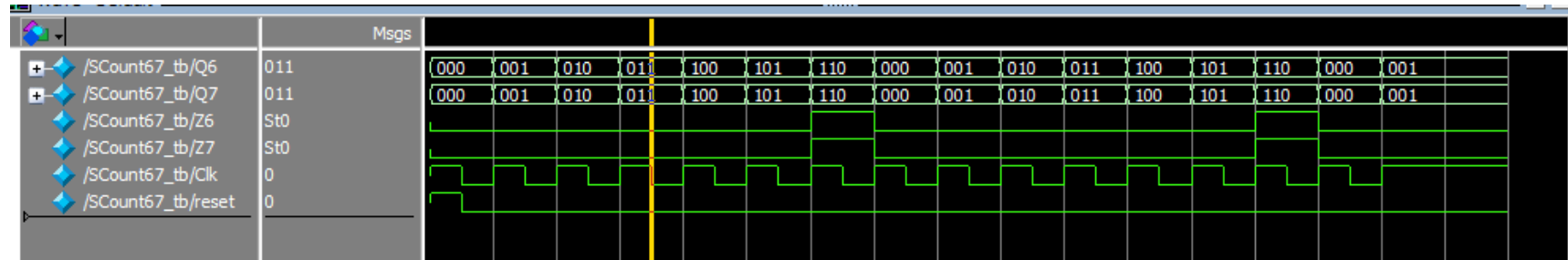
Q7 and Z7 correspond to output for problem 7

```
run
# Time=      10000, Q6=0, Z6=0, Q7=0, Z7=0
run
# Time=      20000, Q6=1, Z6=0, Q7=1, Z7=0
run
# Time=      40000, Q6=2, Z6=0, Q7=2, Z7=0
run
# Time=      60000, Q6=3, Z6=0, Q7=3, Z7=0
run
# Time=      80000, Q6=4, Z6=0, Q7=4, Z7=0
run
# Time=     100000, Q6=5, Z6=0, Q7=5, Z7=0
run
# Time=     120000, Q6=6, Z6=1, Q7=6, Z7=1
run
# Time=     140000, Q6=0, Z6=0, Q7=0, Z7=0
run
# Time=     160000, Q6=1, Z6=0, Q7=1, Z7=0
run
# Time=     180000, Q6=2, Z6=0, Q7=2, Z7=0
run
# Time=     200000, Q6=3, Z6=0, Q7=3, Z7=0
run
# Time=     220000, Q6=4, Z6=0, Q7=4, Z7=0
run
# Time=     240000, Q6=5, Z6=0, Q7=5, Z7=0
run
# Time=     260000, Q6=6, Z6=1, Q7=6, Z7=1
run
# Time=     280000, Q6=0, Z6=0, Q7=0, Z7=0
run
# Time=     300000, Q6=1, Z6=0, Q7=1, Z7=0
run
```



Problem 6 RTL Netlist + Flow Diagram


Compilation Report - SCounter_6		
Flow Summary		
<<Filter>>		
Flow Status	Successful - Tue Feb 20 02:47:44 2024	
Quartus Prime Version	20.1.1 Build 720 11/11/2020 SJ Lite Edition	
Revision Name	SCounter_6	
Top-level Entity Name	SCounter_6	
Family	MAX 10	
Device	10M50DAF484C6GES	
Timing Models	Preliminary	
Total logic elements	5 / 49,760 (< 1 %)	
Total registers	4	
Total pins	6 / 360 (2 %)	
Total virtual pins	0	
Total memory bits	0 / 1,677,312 (0 %)	
Embedded Multiplier 9-bit elements	0 / 288 (0 %)	
Total PLLs	0 / 4 (0 %)	
UFM blocks	0 / 1 (0 %)	
ADC blocks	0 / 2 (0 %)	

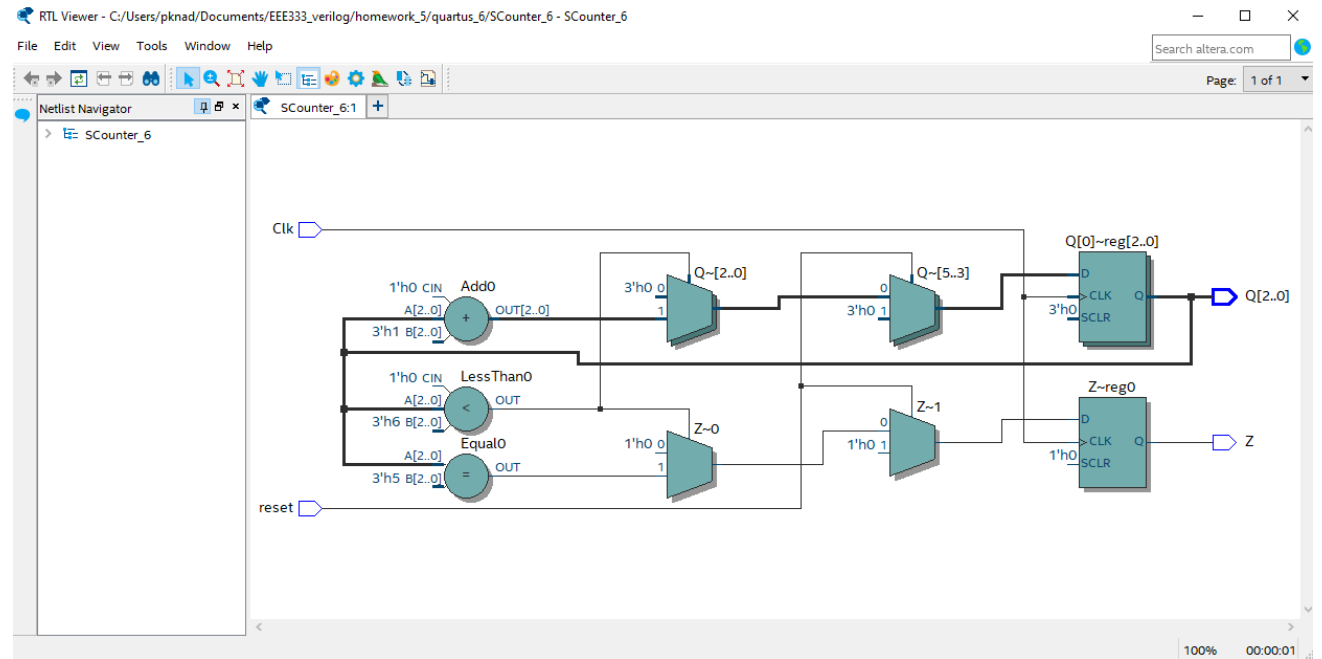

Problem 7 RTL Netlist + Flow Diagram

Compilation Report - SCounter_7	
Table of Contents	
Flow Summary	Flow Summary
Flow Settings	
Flow Non-Default Global Settings	
Flow Elapsed Time	
Flow OS Summary	
Flow Log	
Analysis & Synthesis	
Fitter	
Flow Messages	
Flow Suppressed Messages	
Assembler	
Timing Analyzer	

Flow Status	Successful - Tue Feb 20 02:53:05 2024
Quartus Prime Version	20.1.1 Build 720 11/11/2020 SJ Lite Edition
Revision Name	SCounter_7
Top-level Entity Name	SCounter_7
Family	MAX 10
Device	10M50DAF484C6GES
Timing Models	Preliminary
Total logic elements	5 / 49,760 (< 1 %)
Total registers	3
Total pins	6 / 360 (2 %)
Total virtual pins	0
Total memory bits	0 / 1,677,312 (0 %)
Embedded Multiplier 9-bit elements	0 / 288 (0 %)
Total PLLs	0 / 4 (0 %)
UFM blocks	0 / 1 (0 %)
ADC blocks	0 / 2 (0 %)

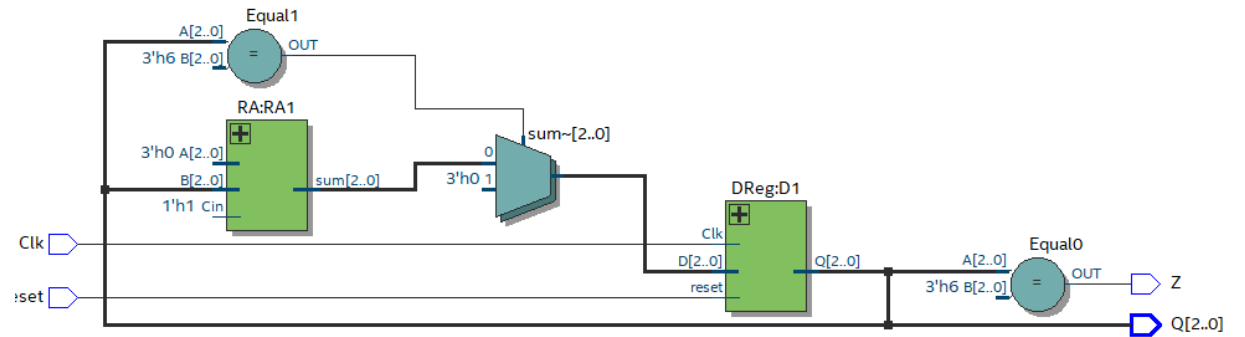

Problem 9 Questions

- a) Some of the differences between the two designs based on the RTL netlist is that the design in problem 6 uses many more muxes and uses its own implementation for the addition. The design from problem 7 uses fewer muxes but relies more heavily from our own implementation of the D Register and the Ripple Adder. Based on the Flow Summary the only difference is the number of registers used Problem 7 uses 1 less than the problem 6 design.
- b) Problem 6 design used 4 registers and the problem 7 design only used 3
- c) Both of the designs used 5 logical elements
- d) I think the design from problem 7 is the best. Not only does it use fewer registers because it relies on our implementation of the ripple adder and D Register we can expect the performance and implementation to be similar across various different types of FPGAs.