

# Homework 6


Pranav Nadimpalli

#### Problem 1 Moore Answers

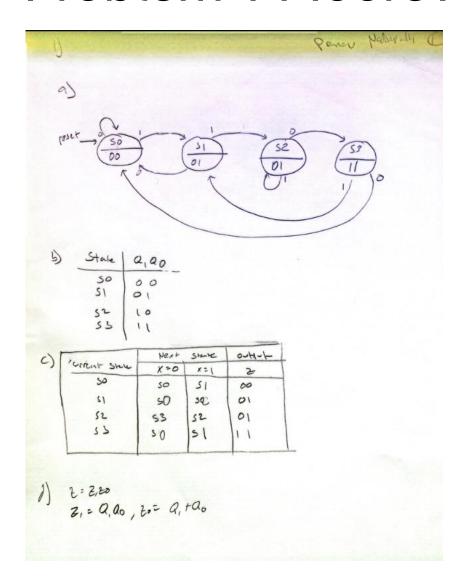


### Problem 2 Wave Forms + Transcript

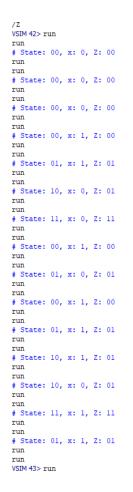

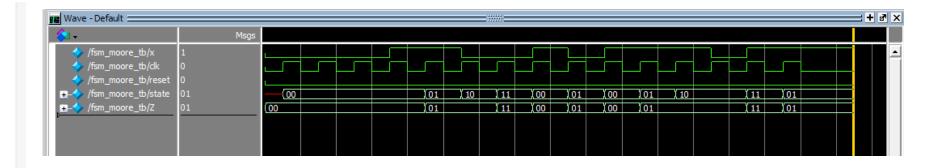


### Problem 2 Moore Flow Summary

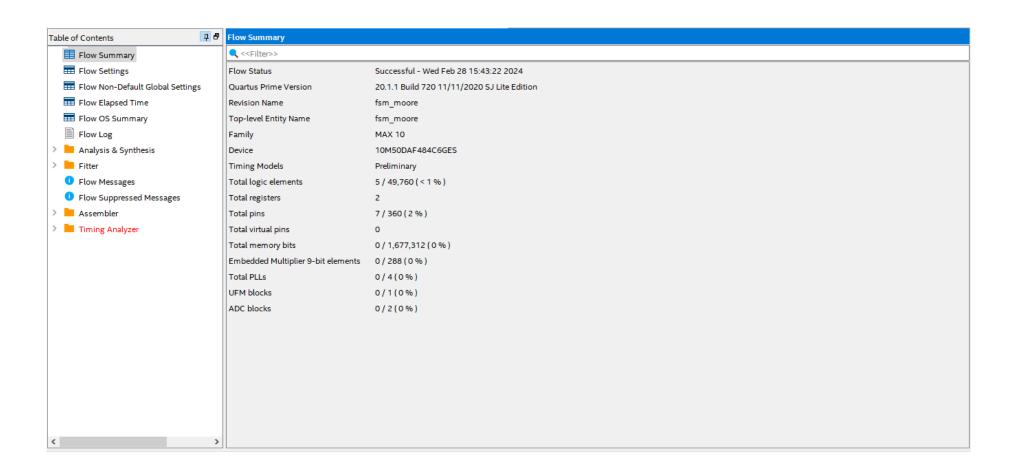

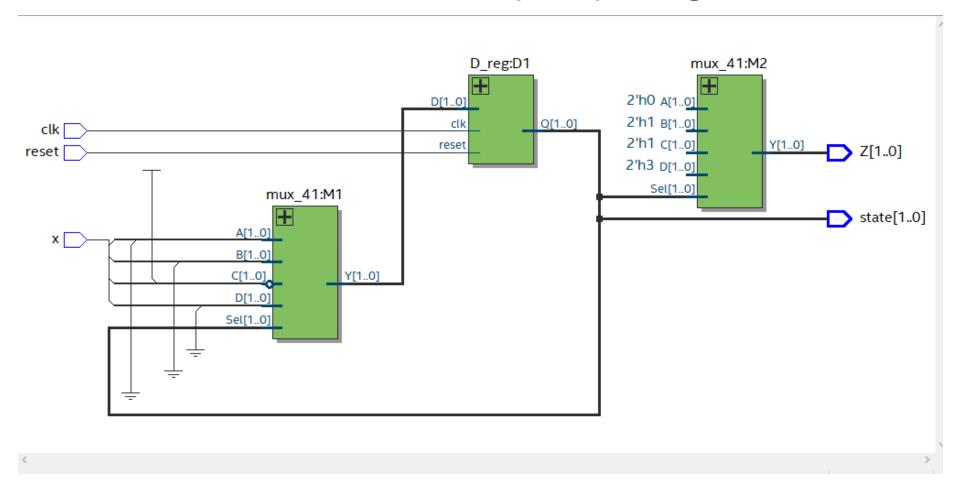
#### Problem 2 Moore Net List

• The main difference is that my output logic is made through a mux



# Problem 3 Mealy Answers

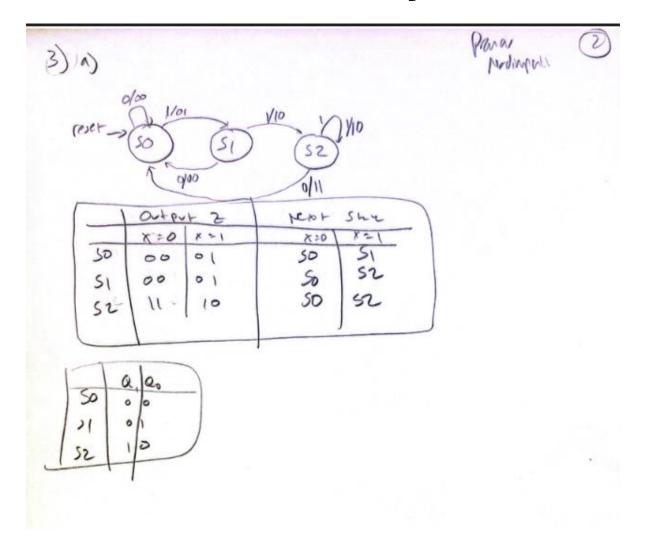


# Problem 3 Mealy Transcript + Waveforms

```
add wave -position end sim:/fsm_mealy_tb/Z
VSIM 21> run
# State: 00, x: 0, Z: 00
run
# State: 00, x: 0, Z: 00
run
# State: 00, x: 0, Z: 00
# State: 00, x: 1, Z: 01
# State: 01, x: 1, Z: 01
# State: 10, x: 0, Z: 11
# State: 00, x: 0, Z: 00
run
run
# State: 00, x: 1, Z: 01
# State: 01, x: 0, Z: 00
run
# State: 00, x: 1, Z: 01
# State: 01, x: 1, Z: 01
# State: 10, x: 1, Z: 10
# State: 10, x: 0, Z: 11
# State: 00, x: 1, Z: 01
# State: 01, x: 1, Z: 01
run
VSIM 22> run
VSIM 22>
```



# Problem 3 Mealy Flow Summary

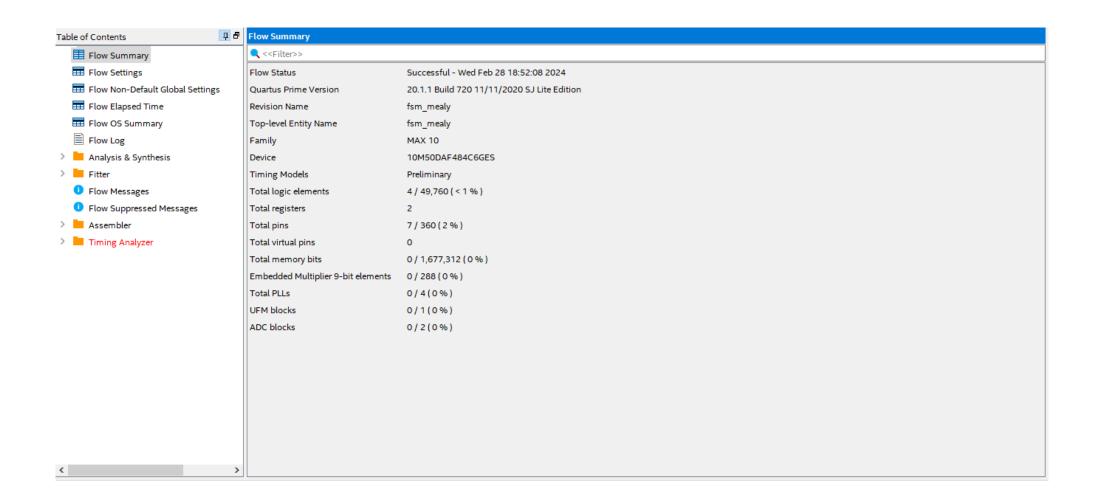

### Problem 3 Mealy Net List

The main difference is that the output calculation involves the input X, and there is one less state in the design which should be expected.

